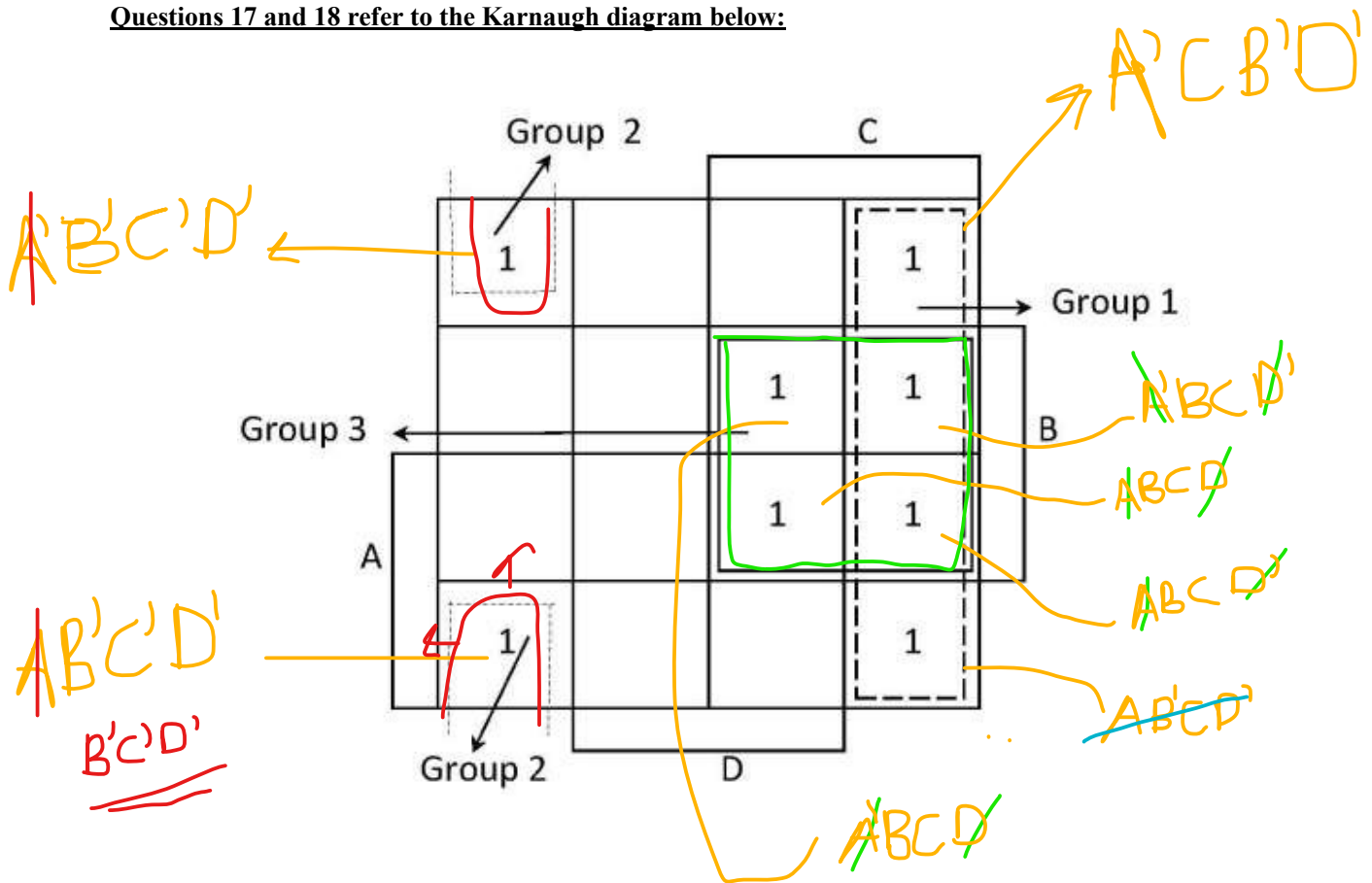








Questions 17 and 18 refer to the Karnaugh diagram below:



**QUESTION 17**

Which term represents Group 1?

1. C
2. D'
3. CD'
4. BCD'

**QUESTION 18**

Which term represents Group 3?

1. BC
2. BD'
3. AB
4. BCD


[TURN OVER]





**QUESTION 20**

Which logic diagram presents the logic expression  $((x \cdot y') \cdot z)'$  ?


1.

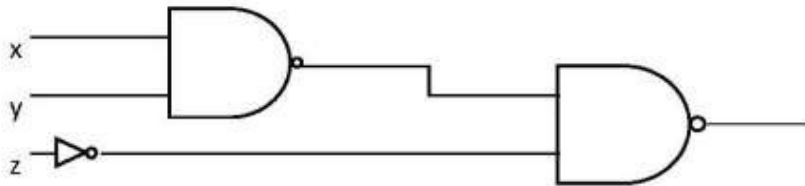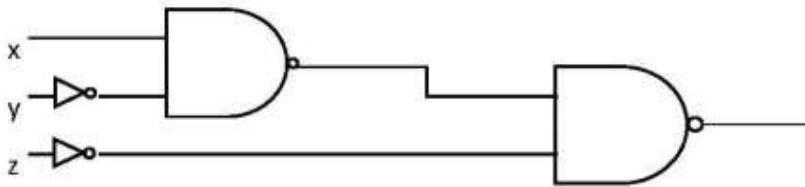


2.




3.

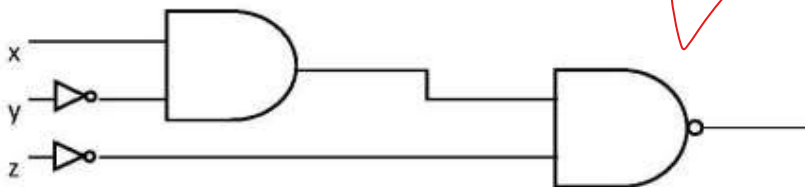

4.

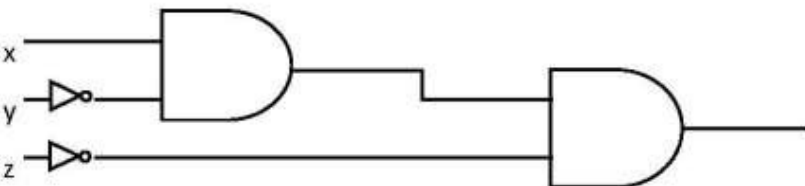**[TURN OVER]**

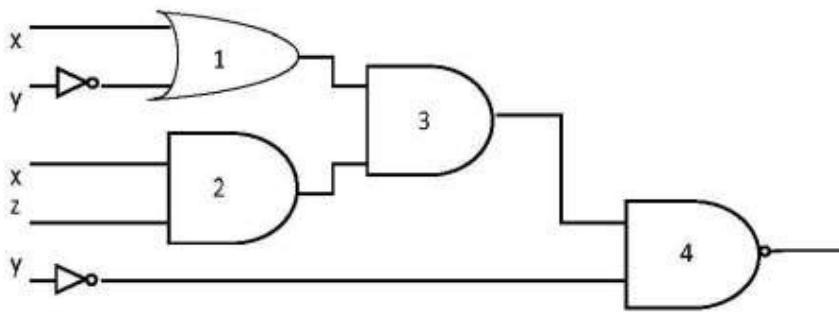**Questions 21, 22 and 23 refer to the following combinational logic circuit:**



$$((x + y') \cdot (x \cdot z)) \cdot y'$$

**QUESTION 21**

Gate 4 is an example of a \_\_\_\_\_ gate.

1. AND ✓✓
2. NAND
3. NOR
4. OR

**QUESTION 22**

What is the output of Gate 3?

1.  $(x + y') \cdot (x \cdot z)$  ✓✓
2.  $(x \cdot y') \cdot (x \cdot z)$
3.  $(x + y') + (x \cdot z)$
4.  $(x \cdot y') + (x \cdot z)$

**QUESTION 23**

What is the output of Gate 4?

1.  $(((x \cdot y') + (x \cdot z)) \cdot y')'$
2.  $(((x + y') + (x \cdot z)) \cdot y')'$
3.  $(((x \cdot y') \cdot (x \cdot z)) \cdot y')'$
4.  $(((x + y') \cdot (x \cdot z)) \cdot y')'$  ✓✓

[TURN OVER]





**Questions 24, 25, 26 and 27 refer to the following scenario:**

A group of students are allowed to have a food stall at the upcoming soccer event at the university, only if they sell all of the following items at their stall:

1. Pancakes
2. Hamburgers
3. Pizzas
4. Chips

Student A can make items 1 and 2. Student B can make items 3 and 4. Student C can make items 2 and 4, and student D can make items 1 and 3.

A Boolean function  $F(A,B,C,D)$  is defined as follows:  $F(A,B,C,D) = 1$  when all 4 items are available (and the food stall is therefore allowed) and  $F(A,B,C,D) = 0$  when all 4 items are not available (and therefore the food stall is not allowed).

Different combinations inputs for A, B, C and D are given in the tables provided in the following FOUR questions. Which alternative shows the correct outputs for F in EACH of the following FOUR questions?

**QUESTION 24**

				Alternative 1	Alternative 2	Alternative 3	Alternative 4
A	B	C	D	F	F	F	F
1	0	0	0	<del>1</del>	0	0	<del>1</del>
0	1	1	0	0	0	<del>1</del>	1

**QUESTION 25**

				Alternative 1	Alternative 2	Alternative 3	Alternative 4
A	B	C	D	F	F	F	F
0	0	1	1	1	<del>0</del>	<del>0</del>	1
1	1	0	0	<del>0</del>	<del>0</del>	1	1

**QUESTION 26**

				Alternative 1	Alternative 2	Alternative 3	Alternative 4
A	B	C	D	F	F	F	F
1	1	0	0	1	<del>0</del>	0	<del>1</del>
0	0	0	1	0	0	1	<del>1</del>

[TURN OVER]