

QUESTION 11Calculate $(1010\ 11)_2 + (101\ 1)_2$

- 1 $(10001\ 01)_2$
- 2 $(10000\ 01)_2$
- 3 $(111101\ 10)_2$
- 4 $(10001\ 10)_2$

Apply Boolean algebra rules to determine the simplest forms of the given Boolean functions in the following **THREE** questions:

QUESTION 12What is the simplest form of the Boolean function $(xy' + 0)'$?

- 1 $x' + y$
- 2 $(xy')' + 0'$
- 3 1
- 4 0

$$\begin{aligned} & (xy' + 0)' \\ &= (\bar{x} + \bar{y}) \\ &= \bar{\bar{x}} + \bar{\bar{y}} \\ &= x + y \end{aligned}$$

QUESTION 13What is the simplest form of the Boolean function $(x + y')x$?

- 1 $y'x$
- 2 $xx + y'x$
- 3 $x + y'$
- 4 x

$$\begin{aligned} & (x + y')x \\ &= x \cdot x + x \cdot y' \\ &= x + x \cdot y' \\ &= y'x \end{aligned}$$

QUESTION 14What is the simplest form of the Boolean function $(x+y+z)'$?


- 1 $x' + y' + z''$
- 2 $x' + y + z$
- 3 $x'y'z''$
- 4 $x'y'z$

$$\begin{aligned} & \overline{(x + y + z)} \\ &= \bar{x} \cdot \bar{y} \cdot \bar{z} \\ &= \bar{x} \cdot \bar{y} \cdot z \end{aligned}$$

[TURN OVER]


QUESTION 16

Consider the following Karnaugh map

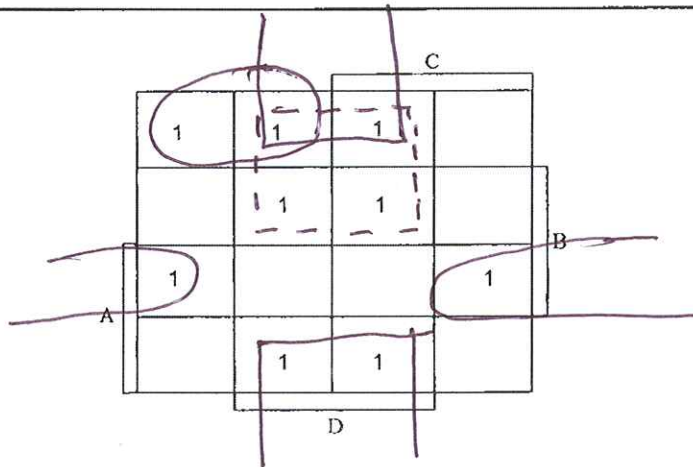


Which one of the following four Karnaugh maps reflects the correct forming of groups?


1

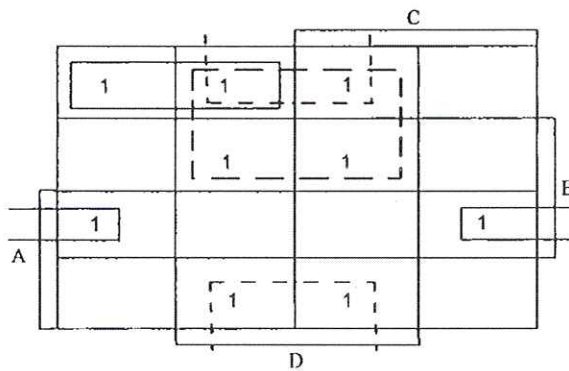

2

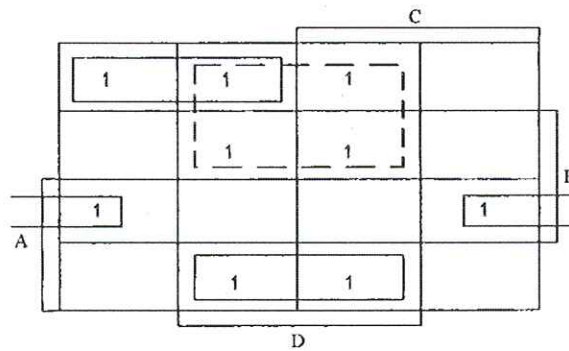

3

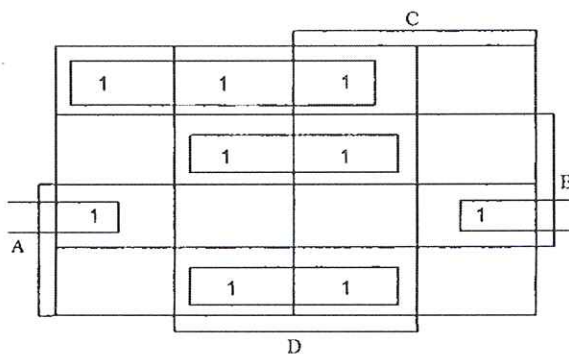

[TURN OVER]

QUESTION 11Calculate $(1010\ 11)_2 + (101\ 1)_2$

- 1 $(10001\ 01)_2$
- 2 $(10000\ 01)_2$
- 3 $(111101\ 10)_2$
- 4 $(10001\ 10)_2$

Apply Boolean algebra rules to determine the simplest forms of the given Boolean functions in the following **THREE** questions:

QUESTION 12What is the simplest form of the Boolean function $(xy' + 0)'$?

- ① $x' + y$
- 2 $(xy')' + 0'$
- 3 1
- 4 0

$$\begin{aligned} & (xy' + 0)' \\ &= (\bar{x} + \bar{y}) \\ &= \bar{\bar{x}} + \bar{\bar{y}} \\ &= x + y \end{aligned}$$

QUESTION 13What is the simplest form of the Boolean function $(x + y')x$?

- ① $y'x$
- 2 $xx + y'x$
- 3 $x + y'$
- 4 x

$$\begin{aligned} & (x + y')x \\ &= xx + xy' \\ &= x + xy' \\ &= y'x \end{aligned}$$

QUESTION 14What is the simplest form of the Boolean function $(x+y+z)'$?


- 1 $x' + y' + z'$
- 2 $x' + y + z$
- 3 $x'y'z''$
- ④ $x'y'z$

$$\begin{aligned} & \overline{(x + y + z)} \\ &= \bar{x} \cdot \bar{y} \cdot \bar{z} \\ &= \bar{x} \cdot \bar{y} \cdot z \end{aligned}$$

[TURN OVER]


QUESTION 16

Consider the following Karnaugh map

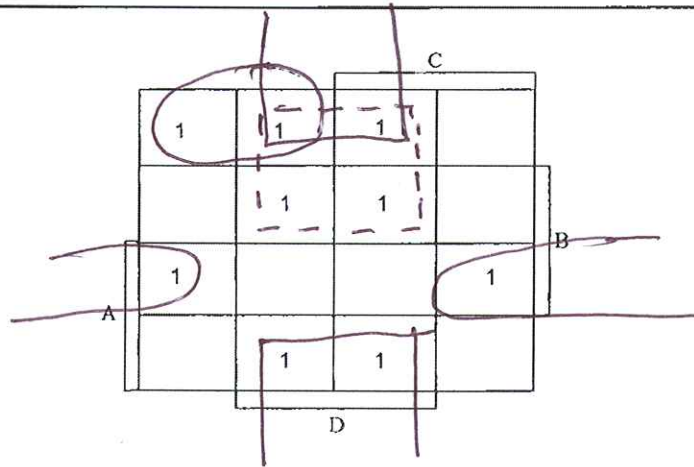


Which one of the following four Karnaugh maps reflects the correct forming of groups?


1

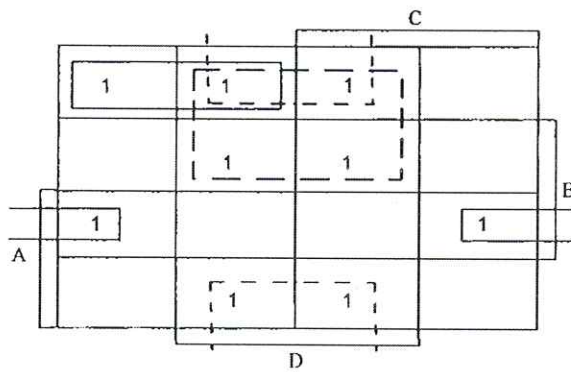

2

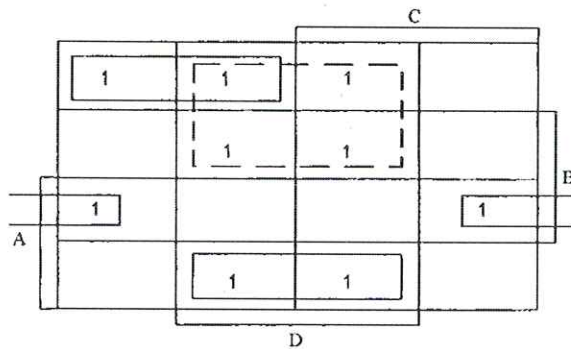


3

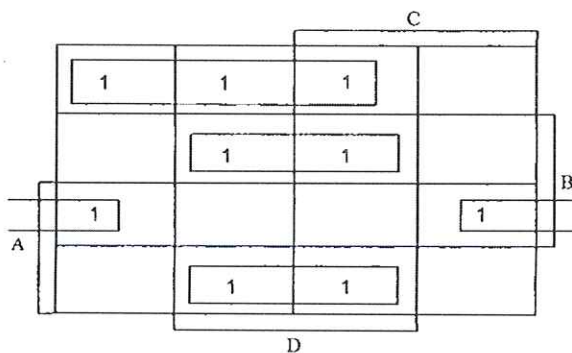

[TURN OVER]

The following FOUR questions refer to the following combinational logic circuit:

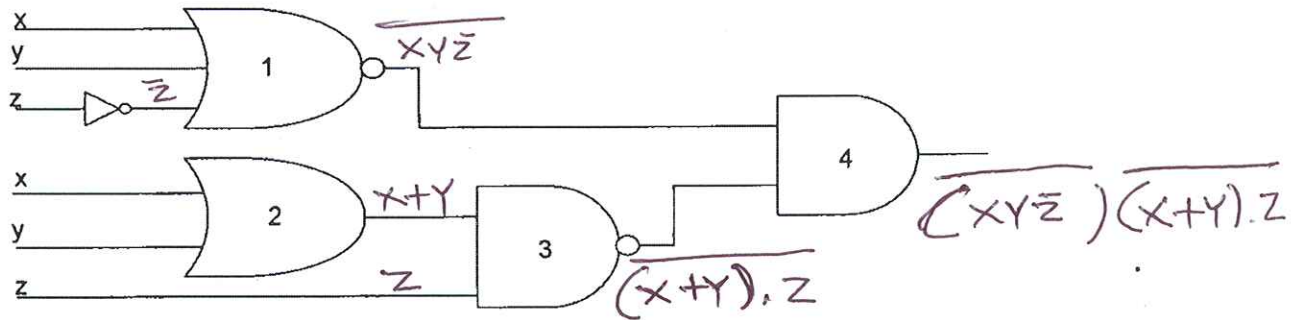

QUESTION 20

What is the output of Gate 1?

- 1 $(x y z)'$
- ② $(x + y + z)'$
- 3 $x + y + z'$
- 4 $x + y$

QUESTION 21

What is the output of Gate 2?

- 1 $x y$
- ② $x + y$
- 3 $(x + y)'$
- 4 $x y z$

QUESTION 22

What is the output of Gate 3?

- 1 $x + y + z$
- 2 $((x y) z)'$
- 3 $((x + y) + z)'$
- ④ $((x + y) z)'$

QUESTION 23

What is the output of Gate 4?


- 1 $(x y z) + ((x + y) + z)'$
- 2 $(x y z) + ((x + y) z)'$
- ③ $(x + y + z)' ((x + y) z)'$
- 4 $(x y z)' ((x + y) z)'$

Rough work

[TURN OVER]


QUESTION 16

Consider the following Karnaugh map

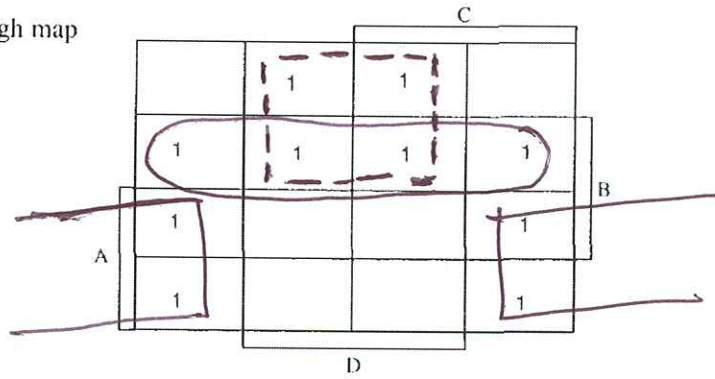


Which one of the following four Karnaugh maps reflects the correct forming of groups?

1

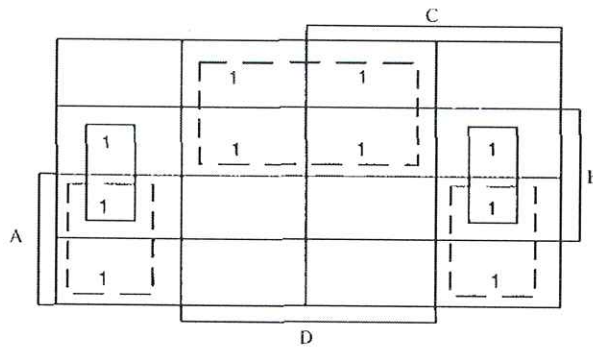


2

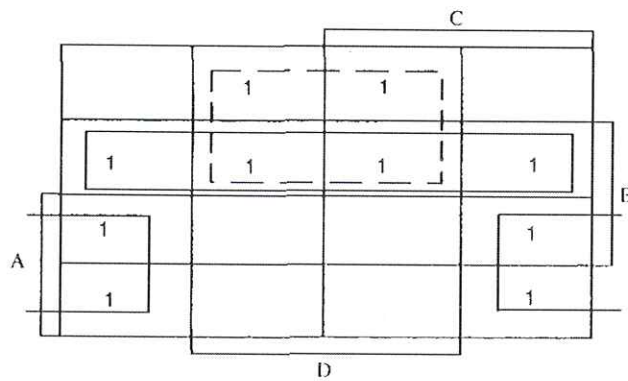

[TURN OVER]

The next FOUR questions refer to the following combinational logic circuit:

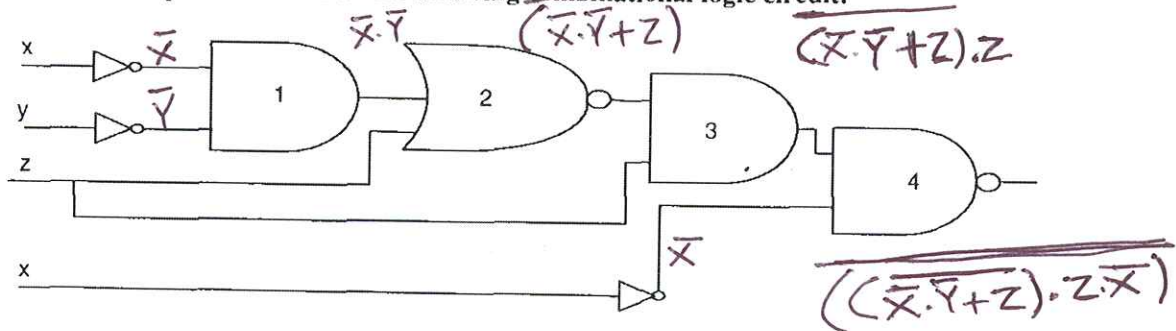

QUESTION 20

What is the output of Gate 1?

- 1 $(x + y)'$
- 2 $x'y'$
- 3 $x' + y'$
- 4 $(xy)'$

QUESTION 21

What is the output of Gate 2?

- 1 $[(x + y)'z]'$
- 2 $(xy)' + z'$
- 3 $(x'y' + z)'$
- 4 $[(x' + y')z]'$

QUESTION 22

What is the output of Gate 3?

- 1 $[(x' + y')z]' + z$
- 2 $[(xy)' + z']z$
- 3 $(x'y' + z)'z$
- 4 $[(x + y)'z]' + z$


QUESTION 23

What is the output of Gate 4?

- 1 $[(x'y' + z)'z]'x'$
- 2 $\{[(x'y' + z)'z]x'\}'$
- 3 $[(x' + y')z]' + z + x'$
- 4 $[(x + y)'z]' + z + x'$

[TURN OVER]

The next THREE questions refer to the Karnaugh map beneath:

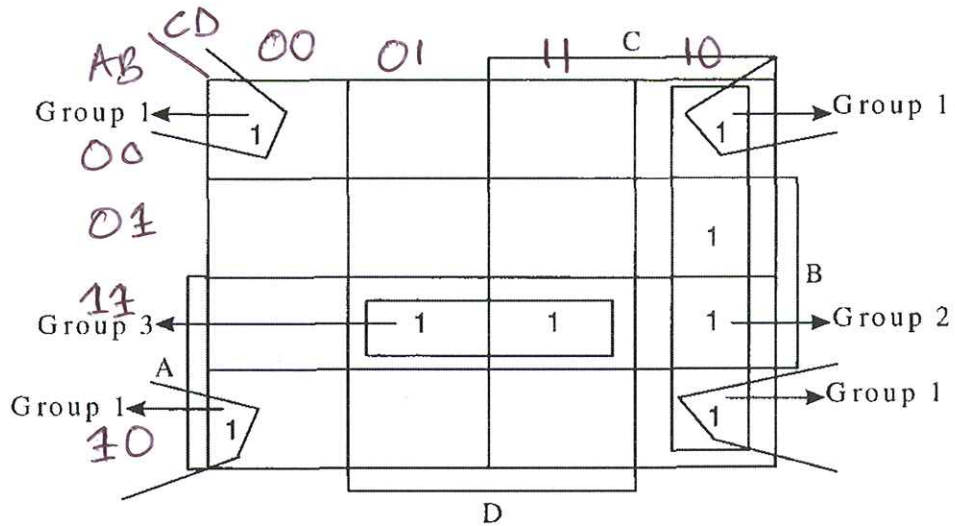

QUESTION 17

Which term represents Group 1?

- 1 $A'B'CD'$
- 2 D'
- 3 A'
- ④ $B'D'$

QUESTION 18

Which term represents Group 2?

- 1 DC'
- 2 C'
- 3 D'
- ④ CD'

QUESTION 19

Which term represents Group 3?

- ① ABD
- 2 AB
- 3 D
- 4 ACD

[TURN OVER]