

Tutorial Letter 203/1/2016

Electromagnetism and Heat

PHY1506

Semester 1

Department of Physics

Solutions to Assignment 03

Bar code

Solutions to compulsory Assignment 03

Question 1

Find first the equivalent resistor for the resistors in parallel, which are $R_1 = 60 \Omega$, $R_2 = 60 \Omega$ and $R_3 = 45 \Omega$. Therefore

$$\begin{aligned} \frac{1}{R_{\text{eq1}}} &= \frac{1}{R_1} + \frac{1}{R_2} + \frac{1}{R_3} \\ &= \frac{1}{60 \Omega} + \frac{1}{60 \Omega} + \frac{1}{45 \Omega} \\ &= \frac{2}{60 \Omega} + \frac{1}{45 \Omega} \\ &= \frac{90 + 60}{60 \times 45} = \frac{150}{2700} \\ R_{\text{eq1}} &= \frac{2700}{150} = 18 \Omega. \end{aligned}$$

This equivalent resistor is now in series with $R_4 = 42 \Omega$. Therefore, $R_{\text{eq2}} = 18 \Omega + 42 \Omega = 60 \Omega$. Finally, R_{eq2} and $R_5 = 40 \Omega$ are in parallel.

$$\begin{aligned} \frac{1}{R_{\text{eq}}} &= \frac{1}{60 \Omega} + \frac{1}{40 \Omega} \\ &= \frac{40 + 60}{240} \\ R_{\text{eq}} &= \mathbf{24 \Omega}. \end{aligned}$$

Question 2

Because the 4Ω resistor is grounded at both ends, the potential difference across this resistor is zero. That is, no current flows through the 4Ω resistor, and the negative terminals of both batteries are at zero potential. To determine the current in the 2Ω resistor, we apply Kirchhoff's loop law. We assume that current I flows clockwise through the 2Ω resistor. Starting from the lower-left corner, the sum of the potential differences across various elements in the circuit is

$$\begin{aligned} +9 - 2I - 3 &= 0 \\ I &= \frac{6 \text{ A}}{2} \\ &= \mathbf{3 \text{ A}} \end{aligned}$$

Question 3

The current through the 10 cm-segment is

$$\begin{aligned} I &= \frac{\varepsilon}{R} \\ &= \frac{15 \text{ V}}{3 \Omega} \\ &= 5 \text{ A}, \end{aligned}$$

which is flowing down. The force on this wire, given by the right-hand rule, is to the right and perpendicular to the current and the magnetic field. The magnitude of the force is

$$\begin{aligned} F &= ILB = 5 \text{ A} \times (0.1 \text{ m}) \times 50 \text{ mT} \\ &= 0.025 \text{ N}. \end{aligned}$$

Therefore, $\vec{F} = (0.025 \text{ N, right})$.

Question 4

The Biot-Savart law for the magnetic field of a current segment $\Delta\vec{s}$ is

$$\vec{B} = \frac{\mu_0}{4\pi} \frac{I\Delta\vec{s} \times \hat{r}}{r^2},$$

where the unit vector \hat{r} points from current segment Δs to the point, a distance r away, at which we want to evaluate the field. For the two linear segments of the wire, $\Delta\vec{s}$ is in the same direction as \hat{r} , so $\Delta\vec{s} \times \hat{r} = 0$. For the curved segment $\Delta\vec{s}$ and \hat{r} are always perpendicular, such that $\Delta\vec{s} \times \hat{r} = \Delta s$. The above equation becomes

$$B = \frac{\mu_0}{4\pi} \frac{I\Delta s}{r^2}.$$

Now we are ready to sum the magnetic field of all the segments at point P . For all segments on the arc, the distance to point P is $r = R$. The superposition of the fields is

$$\begin{aligned} B &= \frac{\mu_0}{4\pi} \frac{I}{R} \int_{\text{arc}} ds \\ &= \frac{\mu_0}{4\pi} \frac{IL}{R^2} \\ &= \frac{\mu_0 I \theta}{4\pi R}, \end{aligned}$$

where $L = R\theta$.

Question 5

The induced emf of the coil is

$$\varepsilon = N \left| \frac{d\Phi}{dt} \right|,$$

where $\Phi = \vec{A} \cdot \vec{B}$. Since \vec{B} is parallel to \vec{A} and $A = \pi r^2$, one obtains

$$\begin{aligned} \varepsilon &= N\pi r^2 \left| \frac{\Delta B}{\Delta t} \right| \\ &= 10^3 \times \pi(0.0050 \text{ m})^2 \left(\frac{0.20 \text{ T}}{10 \times 10^{-3} \text{ s}} \right) \\ &= \mathbf{1.6 \text{ V}} \end{aligned}$$

Question 6

(a) For a point on the axis, $r = 0 \text{ m}$, so $E = 0 \text{ V/m}$.

(b) For a point 2.0 cm from the axis, we have

$$\begin{aligned} E &= \frac{r}{2} \left(\frac{dB}{dt} \right) \\ &= \left(\frac{0.020 \text{ m}}{2} \right) (4.0 \text{ T/s}) \\ &= 40 \text{ mV/m} \end{aligned}$$

Question 7

Since the field is perpendicular to the plane of the loop, \vec{A} is parallel to \vec{B} and $\Phi = AB$. The emf is

$$\begin{aligned} \varepsilon &= \left| \frac{d\Phi}{dt} \right| = A \left| \frac{dB}{dt} \right| \\ &= (0.2 \text{ m})^2 |4 - 4t| \\ &= 0.4 \text{ m}^2 |4 - 4t| = 1.6 |1 - t| \\ I &= \frac{\varepsilon}{R} = \frac{1.6 |1 - t|}{0.10} \\ &= 16(1 - t) \\ t &= 1 \text{ s}, \quad I = 16 \text{ A} \\ t &= 0 \text{ s}, \quad I = 0 \text{ A} \\ t &= 2 \text{ s}, \quad I = -16 \text{ A} \end{aligned}$$

Question 8

The electric field is in the direction of the positive y -axis and the magnetic field is in the direction of the negative z -axis. Substituting into the Lorentz force law, one gets

$$\begin{aligned}
 \vec{F}_{\text{net}} &= q(\vec{E} + \vec{v} \times \vec{B}) \\
 &= 1.6 \times 10^{-19}[-1.0 \times 10^6 \hat{i} + 1.0 \times 10^7 \hat{i}(-0.10\hat{k})] \\
 &= -1.6 \times 10^{-13} \hat{i} + 1.6 \times 10^{-12} \hat{i}(-0.10\hat{k}) \\
 &= -1.6 \times 10^{-13} \hat{i} - 1.6 \times 10^{-13} \hat{i} \times \hat{k} \\
 &= 1.6 \times 10^{-13}(-\hat{i} + \hat{j}) \text{ N.}
 \end{aligned}$$

Thus

$$\begin{aligned}
 F_{\text{net}} &= \sqrt{(1.6)^2 + (1.6)^2} \times 10^{-13} \\
 &= \mathbf{2.26 \times 10^{-13} \text{ N}} \\
 \theta &= \tan^{-1} \left(\frac{1.6 \times 10^{-13}}{1.6 \times 10^{-13}} \right) \\
 &= \mathbf{45^\circ}
 \end{aligned}$$

Question 9

We have that $V_R = IR$ and $V_C = IX_C$, where

$$\begin{aligned}
 X_C &= \frac{1}{\omega C} = \frac{1}{2\pi fC} \\
 &= \frac{1}{2\pi(1.0 \times 10^4)(80 \times 10^{-9})} \\
 &= \mathbf{199 \Omega}.
 \end{aligned}$$

The peak current is

$$\begin{aligned}
 I &= \frac{\varepsilon_0}{\sqrt{R^2 + X_C^2}} \\
 &= \frac{10 \text{ V}}{\sqrt{(199 \Omega)^2 + (150 \Omega)^2}} \\
 &= \mathbf{0.0401 \text{ A}}.
 \end{aligned}$$

Thus,

$$\begin{aligned}
 V_R &= 0.0401 \text{ A} \times 150 \Omega = \mathbf{6.0 \text{ V}} \\
 V_C &= 0.0401 \text{ A} \times 199 \Omega = \mathbf{8.0 \text{ V}}
 \end{aligned}$$

Question 10

(a) The impedance of the circuit is given by

$$Z = \sqrt{R^2 + (X_L - X_C)^2}.$$

For a frequency of 3000 Hz , we have

$$\begin{aligned} X_L &= 2\pi fL = 3000 \text{ Hz} \times 2\pi \times 3 \times 10^{-3} \text{ H} \\ &= 62.20 \Omega \end{aligned}$$

$$\begin{aligned} X_C &= \frac{1}{2\pi \times 3000 \text{ Hz} \times 480 \times 10^{-9} \text{ F}} \\ &= 110.52 \Omega. \end{aligned}$$

Therefore, the impedance is

$$\begin{aligned} Z &= \sqrt{(50 \Omega)^2 + (62.20 \Omega - 110.52 \Omega)^2} \\ &= 69.53 \Omega. \end{aligned}$$

The peak current is

$$\begin{aligned} I &= \frac{\varepsilon_0}{Z} \\ &= \frac{5 \text{ V}}{69.53 \Omega} \\ &= \mathbf{0.072 \text{ A} = 72 \text{ mA}}, \end{aligned}$$

and the phase angle is

$$\begin{aligned} \phi &= \tan^{-1} \left(\frac{X_L - X_C}{R} \right) \\ &= \tan^{-1} \left(\frac{-48.32}{50} \right) \\ &= \mathbf{-4.4^\circ}. \end{aligned}$$

(b) For $f = 4000 \text{ Hz}$, we obtain $Z = 50 \Omega$ and $I = 0.10 \text{ A}$, which gives $\phi = 0.0^\circ$.

(c) For $f = 5000 \text{ Hz}$, we obtain $Z = 62 \Omega$ and $I = 0.08 \text{ A}$, which gives $\phi = 37.0^\circ$.

END